

ENGR 210 / CSCI B441
“Digital Design”

Finite State Machines II

Andrew Lukefahr

Announcements

- P8 – Elevator Controller is out
 - This one is hard.
- P9 – SPI is out
 - This one is new. Might be some changes.

NOLatch

Always specify
defaults for
always_comb!

BLOCKING (=) FOR


always_comb

NON-BLOCKING (<=) for

always_ff

Review: States, Transitions, and Guards

 
~~S₀ + S₁ ⇒ states~~
~~lines ⇒ transitions~~
booleans ⇒ guards
reset ⇒ reset



S_0 & S_1 : are states
two states in this machine
guards: control which transition you take
transitions
→ leaving one state & going to another
(happen @posede clk)

FSM: Traffic Signal Controller

 - A controller for traffic at the intersection of a main highway and a country road.



- The main highway gets priority because it has more cars
 - The main highway signal remains **green** by default.

Traffic signal controller

~~tractors~~


- ~~Cars~~ occasionally arrive from the country road. The traffic signal for the country road must turn **green** only long enough to let the cars on the country road go.
- When no cars are waiting on the country road, the country road traffic signal turns **yellow** then **red** and the traffic signal on the main highway turns **green** again.

There is a sensor to detect cars waiting on the country road. The sensor sends a signal X as input to the controller:

$X = 1$, if there are cars on the country road

$X = 0$, otherwise



What are the 'States'?

 


Moore vs. Mealy Type FSMs

- Thus far we've done "Moore" Type
 - Moore Type: Outputs determined by the state (circle)
- Another technique: "Mealy" Type
 - Mealy Type: Output determined by the transition (arrow)
- Moore: Easier, but more states
- Mealy: Less states, more complicated transitions

Traffic Light: Moore vs. Mealy

  


Mealy Type

 

- Mealy Type:**
- needs less states
 - needs fewer resources to store states
 - is more common in practice


Implementing FSMs with Circuits

 - Encode each state as a number
 - Store this with DFF's
- Generate state transition logic (arrow to next state)
 - Use combinational logic
- Generate output given state + inputs
 - Use combinational logic



State Transition Encoding



| <u>State</u> | <u>X</u> | <u>Next State</u> |
|---------------|----------|-------------------|
| 0 0 (S_0) | 0 | 00 (S_0) |
| 0 0 (S_d) | 1 | 01 (S_1) |
| 0 1 | 0 | 10 (S_2) |
| 0 1 | 1 | 10 (S_2) |
| 1 0 | 0 | 11 (S_3) |
| 1 0 | 1 | 10 (S_2) |
| 1 1 | 0 | 00 (S_0) |
| 1 1 | 1 | 00 (S_0) |

 

Next State Logic


| | <u>State</u> | <u>X</u> | <u>Next State</u> |
|---|--------------|----------|-------------------|
| 0 | 00 | 0 | 00 |
| 1 | 00 | 1 | 01 |
| 2 | 01 | 0 | 10 |
| 3 | 01 | 1 | 10 |
| 4 | 10 | 0 | 11 |
| 5 | 10 | 1 | 10 |
| 6 | 11 | 0 | 00 |
| 7 | 11 | 1 | 00 |

↑↑
 NS_1 NS_0

  


Output Logic (Highway)

| | <u>State</u> | <u>X</u> | <u>H:R</u> | <u>H:Y</u> | <u>H:G</u> |
|---|--------------|----------|------------|------------|------------|
| 0 | 00 | 0 | 0 | 0 | 1 |
| 1 | 00 | 1 | 0 | 1 | 0 |
| 2 | 01 | 0 | 1 | 0 | 0 |
| 3 | 01 | 1 | 1 | 0 | 0 |
| 4 | 10 | 0 | 1 | 0 | 0 |
| 5 | 10 | 1 | 1 | 0 | 0 |
| 6 | 11 | 0 | 1 | 0 | 0 |
| 7 | 11 | 1 | 1 | 0 | 0 |

 


* Simpler methods exist

 

Output Logic (Country Road)


| | <u>State</u> | <u>X</u> | C:R | C:Y | C:6 |
|---|--------------|----------|-----|-----|-----|
| 0 | 00 | 0 | 1 | 0 | 0 |
| 1 | 00 | 1 | 1 | 0 | 0 |
| 2 | 01 | 0 | 1 | 0 | 0 |
| 3 | 01 | 1 | 1 | 0 | 0 |
| 4 | 10 | 0 | 0 | 1 | 0 |
| 5 | 10 | 1 | 0 | 0 | 1 |
| 6 | 11 | 0 | 1 | 0 | 0 |
| 7 | 11 | 1 | 1 | 0 | 0 |

* Simpler methods exist

 

State Machine to Verilog

- Define states?

 


```
enum { ST_0, ST_1, ST_2, ST_3 } state, nextState;
```

State Machine to Verilog

```
always_ff @ (posedge clk) begin
    if (rst) state <= ST_0;
    else state <= nextState;
end

 
always_comb begin
    nextState = state; //default
    case(state)
        ST_0: nextState = ST_1; //goto state 1
        ST_1: nextState = ST_2;
        ST_2: nextState = ST_3;
        ST_3: nextState = ST_0; //loop
        default: nextState = ST_0; //just in case
    endcase
end
```



State Machine to Verilog

- What is this missing?

 
```
always_comb begin
    nextState = state; //default
    case(state)
        ST_0:
            if (x) nextState = ST_1;
        ST_1:
            nextState = ST_2;
        ST_2:
            if (~x) nextState = ST_3;
        // ST_3 and default cases
    endcase
end
```



State Machine to Verilog


- What else is this missing?
 
```
always_comb begin
    nextState = state; //default
    case(state)
        ST_0:
            if (X) nextState = ST_1;
            // ST_1-3 and default cases
    endcase
end
```



State Machine to Verilog

```
always_comb begin
    nextState = state; //default
    Hryg = {0,0,1}; Cryg={1,0,0};
    case(state)
        ST_0: begin
            if (X) begin
                nextState = ST_1;
                Hryg = {0,1,0};
                Cryg = {1,0,0}; //optional
            end else begin
                nextState = ST_0; //optional
                Hryg = {0,0,1}; //optional
                Cryg = {1,0,0}; //optional
            end
        end
        // ST_1-3 and default cases
    endcase
end
```

 

```

module traffic(
    input clk,
    input rst,
    input x,
    output logic [2:0] Hryg, //red-yellow-green
    output logic [2:0] Cryg //red-yellow-green
);

enum { ST_0, ST_1, ST_2, ST_3 } state,
nextState;

always_ff @(posedge clk) begin
    if (rst) state <= ST_0;
    else      state <= nextState;
end

always_comb begin
    nextState = state; //default
    Hryg = 3'b001; Cryg = 3'b100;

    case (state)

        ST_0: begin
            if (x) begin
                nextState = ST_1;
                Hryg = 3'b010;
                Cryg = 3'b100; //opt
            end else begin //opt
                nextState = ST_0; //opt
                Hryg = 3'b001; //opt
                Cryg = 3'b100; //opt
            end
        end
    end

```

```

        ST_1: begin
            nextState = ST_2;
            Hryg = 3'b100;
            Cryg = 3'b100; //opt
        end

        ST_2: begin
            if (x) begin
                nextState = ST_2;
                Hryg = 3'b100;
                Cryg = 3'b001;
            end else begin
                nextState = ST_3;
                Hryg = 3'b100;
                Cryg = 3'b010;
            end
        end

        ST_3: begin
            nextState = ST_0;
            Hryg = 3'b100;
            Cryg = 3'b100; //opt
        end
    endcase
end

endmodule

```

```
`timescale 1ns / 1ps

module traffic_tb();

logic clk;
logic rst;
logic x;
wire [2:0] Hryg;
wire [2:0] Cryg;

traffic t0( .clk, .rst, .x, .Hryg, .Cryg);

always #10 clk = ~clk;

initial begin
    clk = 0; rst = 1; x=0;
    @ (negedge clk);
    @ (negedge clk);
    rst = 0;
```


```
@ (negedge clk);
@ (negedge clk);

x = 1;
@ (negedge clk);
@ (negedge clk);
@ (negedge clk);

x = 0;
@ (negedge clk);
@ (negedge clk);
@ (negedge clk);

$finish;
end
endmodule
```

Testbenches for State Machines

 

- Outputs change @posedge clk
- Change Inputs @negedge clk

Your Turn

- Build a digital safe / keypad lock
- The user must enter the digits 5 – 4 – 3 in that order to unlock the door. Any other inputs result in a locked door.
- Once unlocked, the door remains unlocked until E key pressed. *Ignore all other keys while unlocked.*



should unlock : 5 - 5 - 4 - 3, 5 - 4 - 5 - 4 - 3

- Draw the state machine!


Lock State Machine

- Recall: 5 - 4 - 3
- E: relock



State Machine in Verilog
 
```
module Lock(  
    input clk, rst,  
    input [9:0] num,  
    input e, //relock  
    output unlock  
) ;
```




State Machine in Verilog

```
module Lock(
    input clk, rst,
    input [9:0] num,
    input e, //relock
    output unlock
);
```

```
enum {ST_IDLE, ST_5, ST_4, ST_UL } state, next_state;
```

 
```
//seq logic
always_ff @(posedge clk) begin
    if (rst) state <= ST_IDLE;
    else      state <= next_state;
end
```



State Machine in Verilog


```
//comb logic block  
always_comb begin
```

```
end
```

 


State Machine in Verilog
 
```
//comb logic block
always_comb begin
    next_state = state; //default
    unlock = 1'h0; //default
    case (state)
        ST_IDLE:
            if (num[5]) next_state = ST_5;
        ST_5:
            if (num[4]) next_state = ST_4;
        ST_4:
            if (num[3]) next_state = ST_UL;
        ST_UL: if (e)
            next_state = ST_IDLE;
    endcase
end
```



State Machine in Verilog

 
```
case (state)
    ST_IDLE:
        if (num[5])
            next_state = ST_5;
    ST_5: begin
        if (num[4])
            next_state = ST_4;
    end
    ST_4: begin
        if (num[3])
            next_state = ST_UL;
    end
endcase
```



```
end
ST_UL: begin
    if (e)
        next_state = ST_IDLE;
    end
endcase
```

State Machine in Verilog

```
case (state)
    ST_IDLE:
        if (num[5])
            next_state = ST_5;
    ST_5: begin
        if (num[4])
            next_state = ST_4;
        else if (num[5])
            next_state = ST_5;
        else if ((|num) | e) //other btns
            next_state = ST_IDLE;
    end
    ST_4: begin
        if (num[3])
            next_state = ST_UL;
```

 


```
        else if (num[5])
            next_state = ST_5;
        else if ( (|num) | e) // other btns
            next_state = ST_IDLE;
    end
    ST_UL: begin
        unlock = 1'h1;
        if (e)
            next_state = ST_IDLE;
    end
endcase
```

Timing



Flip-Flop Timing

 - What's the delay for this Latch?
- Assume 5ps/ gate
- What about a Flip-Flop?




Flip-Flop Timing


- Assume 5ps/ Gate

  

Glitch

 

 Results in a short low-going pulse at the output of N_2 with length approximately equal to the propagation delay through N_1 .




Setup and Hold Time

- **Setup Time:** minimum time the inputs to a flip-flop must be stable before the clock edge
- **Hold Time:** minimum time the inputs to a flip-flop must be stable after the clock edge

Setup Time

Setup/Hold Time

 


Inter Flip-Flop Timing

Intra Flip-Flop Timing

Intra Flip-Flop Timing

Register to register timing:

 - output of a register $Q1$
- some combinational circuit
- input to the next register $D2$




Delays:

- t_{co} , clock to output delay,
- t_{pd} , propagation delay in combinational circuit
- t_c , clock period

Timing requirement:


$$t_{co} + t_{pd} + t_{su} < t_c$$

 

Slack

- Extra time between combinational propagation delay and setup time
- Time between stable input to Flip-Flop and next clock edge

 - Vivado:
 - WNS: Worst-case Negative Slack



- If this number is <0, your circuit will (probably) not work

Next Time

- Communication